

Index

A

Accumulator
 load and output instructions, 11–25
 logic instructions, 11–30
 operations, 9–10–9–13
 shifting bits in, 11–42

Adding Numbers, 11–34

Agency Approvals, 2–7

Auxiliary Functions, 3–17

B

Bases
 expansion, 4–14
 I/O supported, 4–8
 installation spacing, 2–4
 installing modules, 2–10
 local, 4–14
 mounting dimensions, 2–10, 4–8
 power budget, 4–26–4–31
 power specifications, 2–6
 power supply schematics, 4–11
 power wiring, 2–11
 run relay, 4–12
 setting base jumpers, 4–16
 setting switches, 4–16
 specifications, 4–10–4–13

Battery, replacement, 3–14, 13–2

Baud Rate, 3–12

Bit Operation Instructions, 11–42

Boolean Instructions, 9–3, 11–4–11–18

C

Communication, instructions, 11–52

Communication Port
 data format, 3–13
 DL340, 3–12
 DL340 port diagrams, 3–13
 master / slave selection, 3–13
 response delay time, 3–13

Comparative Boolean Instructions, 11–19–11–21
 in stages, 10–18, 12–12–12–19

Configuration, I/O examples, 4–17–4–25

Control Relays, 8–21

Converting Number Formats, 11–44–11–49

Counters, 8–22, 9–9, 11–23
 in stages, 10–15, 12–19

CPU
 auxiliary functions, 3–17
 battery, 3–14
 clearing memory, 3–21
 features, 3–2
 indicators, 13–3–13–6
 memory options, 3–5
 mode setting, 8–4
 modes of operation, 3–20, 8–6–8–8
 operating system, 8–3
 scan time, 8–16
 setup
 DL330/DL340P, 3–9
 DL340, 3–10
 DL340 network address, 3–12
 setup and system functions, 3–16
 specifications, 3–3
 switches
 DL330/DL330P, 3–9
 DL340, 3–10–3–13

D

- Data Instructions, 9–12–9–47
 - in stages, 10–17
- Data Registers, 8–23
- Derating Characteristics, 5–10
- Dimensions, 2–7
- Discrete Input
 - specifications, 6–4–6–15
 - terminology, 6–2
- Discrete Memory, 8–19
- Discrete Output
 - specifications, 7–6–7–20
 - terminology, 7–2
- Dividing Numbers, 11–40

E

- EEPROM, 3–5
- Enclosures, selection, 2–7
- End Instruction, 9–3
- Environmental Specifications, 2–6
- Error Codes, B–2
- Execution Times, 8–18, C–2–C–9
- Expansion Bases, 4–14–4–15

F

- Fault Messages, 11–56
- Flowchart Programming, 10–26
- Forcing I/O, 8–10
- Fuses
 - I/O protection, 5–12
 - power supply, 13–4

G

- Grounding, 2–4

I

- I/O Memory, 8–20
- I/O Modules
 - address switch (base), 4–16

- configuration history, 4–2
- derating, 5–10
- discrete input specifications, 6–4–6–15
- discrete output specifications, 7–6–7–20
- example configurations, 4–17–4–25
- fuse protection, 5–12–5–15
- installing, 4–13
- numbering, 4–2, 4–3
- placement, 4–4–4–6
- point requirements, 4–3
- power requirements, 4–27–4–29
- response time, 8–14
- selection considerations, 5–2
- sinking and sourcing circuits, 5–2
- solid state field devices, 5–9
- testing outputs, 13–8
- troubleshooting, 13–10
- update sequence, 8–8
- wiring guidelines, 2–12, 5–11

- Indicators, CPU, 13–3–13–6

- Input Modules
 - specifications, 6–4–6–15
 - wiring diagrams, 6–4–6–15

- Installation
 - base mounting dimensions, 2–10
 - base power wiring, 2–11
 - base wiring, 4–7–4–9
 - component dimensions, 2–7
 - DL330/DL330P setup, 3–9
 - DL340 setup, 3–10
 - grounding, 2–4
 - I/O modules, 4–13
 - I/O wiring guidelines, 2–12
 - installing modules, 2–10
 - local and expansion bases, 4–14
 - panel design specifications, 2–4
 - setting CPU switches, 3–9–3–12

- Instruction, execution times, 8–18, C–2–C–9

- Instruction Set, index, 11–3

- Instructions
 - accumulator load and output, 11–25
 - accumulator logic instructions, 11–30
 - bit operations, 11–42
 - boolean, 11–4–11–18
 - comparative boolean, 11–19–11–21
 - in stages, 12–12–12–19

- counters, 11–23
 - in stages, 12–19
- end placement, 9–3, 13–13
- initial stage, 12–3
- jump, 12–5
- math, 11–34
- messages (fault), 11–56
- network communication, 11–52
- not jump, 12–5
- number conversion, 11–44
- program control, 11–50
- RLL^{PLUS}, 12–2
- shift registers, 11–24
 - in stages, 12–21
- stage, 12–3
- timers, 11–22
 - in stages, 12–18

J

- Jump Instruction, 12–5
- Jumpers, on bases, 4–16

L

- Latching Outputs, in stages, 10–14
- Local Bases, 4–14

M

- Maintenance
 - battery replacement, 13–2
 - guidelines, 13–2
- Master Control Relays, 11–50
- Math Instructions, 11–34
- Memory
 - battery backup, 3–14
 - clearing, 3–21
 - external storage, 3–4–3–6
 - initialization, 8–5
 - maps, 8–19, 8–25–8–37
 - options for CPUs, 3–4–3–6
 - PROM Writer Unit, 3–6
 - retentive, 3–4, 3–11, 8–5
 - retentive selection switch, 3–9
 - volatile and non-volatile, 3–4
- Messages, 11–56
- Multiplying Numbers, 11–38

N

- Network Address, 3–12, 3–13
- Network Instructions, 11–52
- Noise, reducing problems, 13–11
- Not Jump Instruction, 12–5
- Number Conversion Instructions, 11–44

O

- Output Modules
 - specifications, 7–6–7–20
 - using outputs in stages, 10–12
 - wiring diagrams, 7–6–7–20

P

- Pause Relay, 13–13
- Power Budget, 4–26–4–31
 - worksheet, 4–31
- Power Specifications, 2–6
- Power Supply
 - schematics, 4–11
 - wiring, 4–9–4–12
- Program Control Instructions, 11–50
- Program Mode, 8–6
- Programming
 - accumulator usage, 9–10–9–12
 - basic concepts, 9–2
 - counters, 9–9
 - device connections, 3–18
 - flowchart style, 10–26
 - instruction set index, 11–3
 - RLL PLUS concepts, 10–2–10–37
 - stack operation, 9–6
 - timers, 9–8
 - troubleshooting, 13–12
- PROM Writer Unit, 3–6

Q

- Quick Start, A–2–A–7

R

- RAM, 3–5
- Retentive Memory, 3–4, 3–11
 - initialization of, 8–5
 - selection switch, 3–9
- Run Mode, 8–7
- Run Relay, 4–12

S

Safety

- fuses, 5–12
- guidelines, 2–2
- levels of protection, 2–2
- panel design specifications, 2–4
- planning for, 2–2
- sources of assistance, 2–2

Scan Time, 8–16

Shift Registers, 8–24, 11–24
in stages, 12–21

Shifting Accumulator Bits, 11–42

Sinking Circuits, 5–2

Sourcing Circuits, 5–2

Special Registers, 8–24

Special Relays, 8–24
using the pause relay, 13–13

Specifications

- base power, 2–6
- CPU, 3–3
- discrete input modules, 6–4–6–15
- discrete output modules, 7–6–7–20
- environmental, 2–6
- panel design, 2–4
- power source, 2–6

Stages, 8–23

- activating, 10–8
- activating with power flow, 10–11
- execution rules, 10–7
- flowchart view, 10–26
- instructions, 12–3
- numbering, 10–6
- parallel branching concepts, 10–19
- resetting stages, 12–11
- setting, 10–10
- setting stages, 12–11
- unusual operations, 10–24
- using bits as contacts, 10–22, 12–7–12–10
- using comparative boolean in, 10–18
- using data instructions in, 10–17
- using initial, 10–8
- using outputs in, 10–12
- using to latch outputs, 10–14
- using with jump instructions, 10–9

Storing Programs, 3–4–3–8

Subtracting Numbers, 11–36

Switches, CPU

- DL330/DL330P, 3–9
- DL340, 3–10

DL340 communication, 3–12

System

- component dimensions, 2–7
- components, 1–4
- enclosures, 2–7
- environmental specifications, 2–6
- operation, 8–2–8–37
- panel design specifications, 2–4
- power supply requirements, 2–6

T

Terminology

- discrete input, 6–2
- discrete output, 7–2

Timers, 8–22, 9–8, 11–22
in stages, 10–15, 12–18

Troubleshooting

- See also Indicators
- I/O modules, 13–10
- noise problems, 13–11
- programs, 13–12
- testing outputs, 13–8

U

UVPROM, 3–5

- comparing to the CPU, 3–8
- copying CPU program to, 3–7
- erasing, 3–8
- installing in CPU, 3–9, 3–10
- loading program to CPU, 3–8

W

Weights, D–2

Wiring

- base power, 2–11
- bases, 4–7–4–9
- I/O guidelines, 5–11
- I/O modules, 2–12
- run relay, 4–12

Word Memory, 8–19